

## HW2 Solutions [9 problems, 64 points]

Covers lectures L4 – L5

Due: 18 September 2023

### Drill Problems [28 points]


1. [12 points, Lecture 5] Write a SystemVerilog module and testbench for each of the following components.

See `hw2library.sv` on Canvas. As you can guess from that filename, you will be adding more stuff to your `library.sv` file over future homework assignments.

2. [6 points, Lecture 4] Sketch a schematic of the circuit described by the following SystemVerilog code. Do not simplify:

```
module hw2prob2
  (output logic e, f,
   input  logic a, b, c);

  assign e = a & (b | c);
  assign f = ~ (a | b);
```

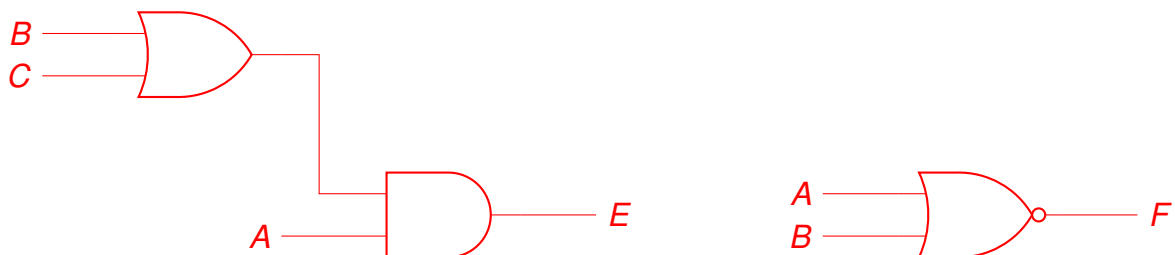

3. [4 points, Lecture 4] Using *procedural* SystemVerilog, write a module that computes a four-input XOR function. The module has a 4-bit input **a**, and output **y**.

`hw2prob3.sv` has been posted to Canvas.

4. [6 points, Lecture 4] Using *procedural* SystemVerilog, write a module called **Minority**. The module's output is a one only if more than half of its inputs are zero.

`hw2prob4.sv` has been posted to Canvas.

## Non-Drill Problems [36 points]

5. [8 points, Lecture 5] Use an 8:1 multiplexer module to implement  $F(A,B,C,D) = A'B'CD + A'B + ABD + A(B'CD' + C'D)$ .

**hw2prob5.sv is posted on Canvas.**

6. [12 points, Lecture 5] Let's test Shannon's Expansion Theorem. Here is a 6-input function:

**hw2prob6.sv is posted on Canvas.**

7. [4 points, Lecture 4] Write a SystemVerilog module that receives as input a year number, **year**, and produces an output, **leap4**, that is one if the year is evenly divisible by 4 (i.e., the remainder is 0), and zero otherwise. Assume that valid years are zero through 2040, inclusive.

**hw2prob7.sv has been posted to Canvas.**

8. [4 points, Lecture 4] But, wait a minute! If you know about leap years, you probably know that the "divide by four" definition is not quite correct. A year is a leap year if:

- (a) The year is evenly divisible by four
- (b) except in the case where it is evenly divisible by 100 and thus is not a leap year,
- (c) except in the case where it is evenly divisible by 400 and thus is a leap year.

Your answer to the last problem only followed rule #1. Implement a better version, using the following header, to correctly determine if a year is, in fact, a leap year. You may use your module from the last problem to implement this newer version, but if you do, please include a copy in your file submission.

**hw2prob8.sv has been posted to Canvas.**

9. [8 points, Lecture 4] After all this talk about not dividing in the previous problems, let's go ahead and build a very simple divider.

Develop a minimized Boolean implementation of a 2-bit divider. The system has 2-bit inputs **AB** (dividend) and **CD** (divisor), and generates 2-bit outputs, **EF** (quotient), and **GH** (remainder).

(a) Draw the truth table for E, F, G, and H.

AB	CD	EF	GH
00	00	xx	xx
00	01	00	00
00	10	00	00
00	11	00	00
01	00	xx	xx
01	01	01	00
01	10	00	01
01	11	00	01
10	00	xx	xx
10	01	10	00
10	10	01	00
10	11	00	10
11	00	xx	xx
11	01	11	00
11	10	01	01
11	11	01	00

(b) Minimize the four output functions.

AB \ CD	CD			
	00	01	11	10
00	X			
01	X			
11	X	1		
10	X	1		

$$E = A\overline{C}$$

AB \ CD	CD			
	00	01	11	10
00	X			
01	X	1		
11	X	1	1	1
10	X			1

$$F = B\overline{C} + AB + A\overline{D}$$

AB \ CD				
	00	01	11	10
00	X			
01	X			
11	X			
10	X		1	

$$G = \overline{A}BCD$$

AB \ CD				
	00	01	11	10
00	X			
01	X		1	1
11	X			1
10	X			

$$H = B\overline{D} + \overline{A}BC$$

(c) and (d) The code is posted to Canvas. Note the testbench (you did write a testbench, right?) which instantiates both modules and compares the outputs of each.